


Computer Architecture HW7

MEVS-SA K016

11/7/2024

$$\begin{array}{r} 01 = + \\ - 00 \\ \hline 11 \end{array}$$

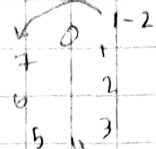1 1 ← carry in
1 1 1 becomes signed 5 11 3



$$\begin{array}{r} 100 \\ 01 \\ \hline 001 \end{array}$$

carry out

$$\begin{array}{r} 010 \\ - 001 \\ \hline 001 \end{array}$$

Find $a < b$

when $a < b$, there is no carry out bit

when $a > b$, there is a carry out bit


Therefore $out = c_out$ (before edge cases)

ALU

Overflow: addition and subtraction

$a[31] \ b[31] \ result[31]$
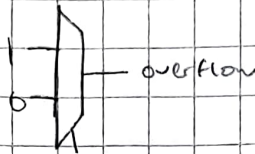
$$\begin{array}{l} 1+1=0 \ (-)+(-) = +? \ \text{overflow} = 1 \\ 0+0=1 \ (+)+(+) = -? \ \text{overflow} = 1 \\ 1+1=1 \ (-)+(-) = -? \ \text{overflow} = 0 \\ 0+0=0 \ (+)+(+) = +? \ \text{overflow} = 0 \end{array}$$



$$a[31] \cdot b[31] \ result[31]$$

equal: $a == b$

xor: check if same

$$0 \oplus 0 = 0 \quad 1 \oplus 1 = 0 \quad \text{if equal}$$

Unary/bitwise

$$\begin{array}{l} 1 \& 1 \& 1 \dots \& 1 = 1 \\ 0 \& 0 \& 0 \dots \& 0 = 0 \\ 0 \& 1 \& 0 \dots \& 1 = 0 \end{array}$$

Zero:

result


Unary/bit-wise operator!

$$000 \dots 000 \Rightarrow \& (result[N-1:0])$$

(results are flipped with results)

Shifters

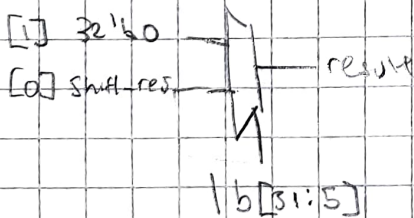$b[31:5] \rightarrow$ goes down and checks if any other bits are 1



SHF \rightarrow overflow
add \rightarrow + overflow
else \rightarrow 0